
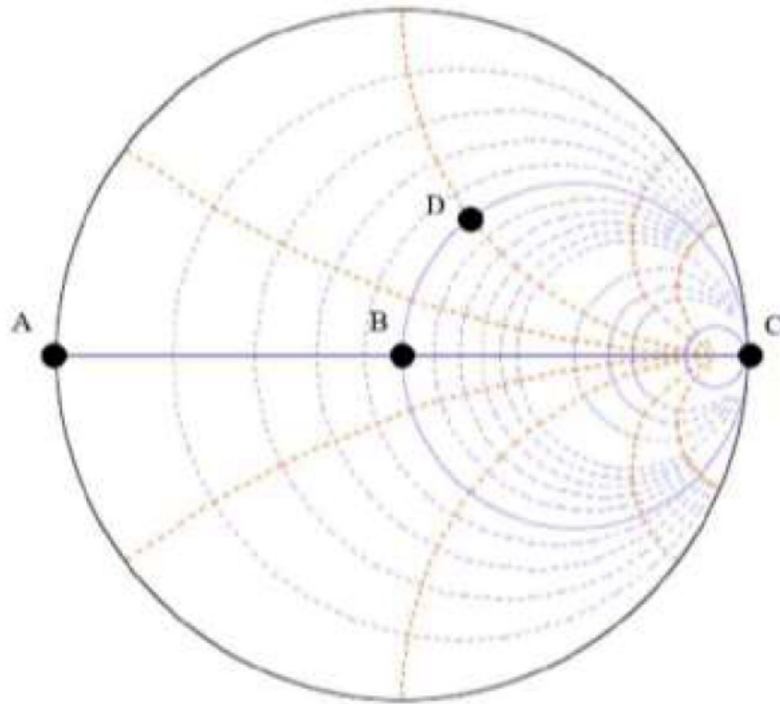


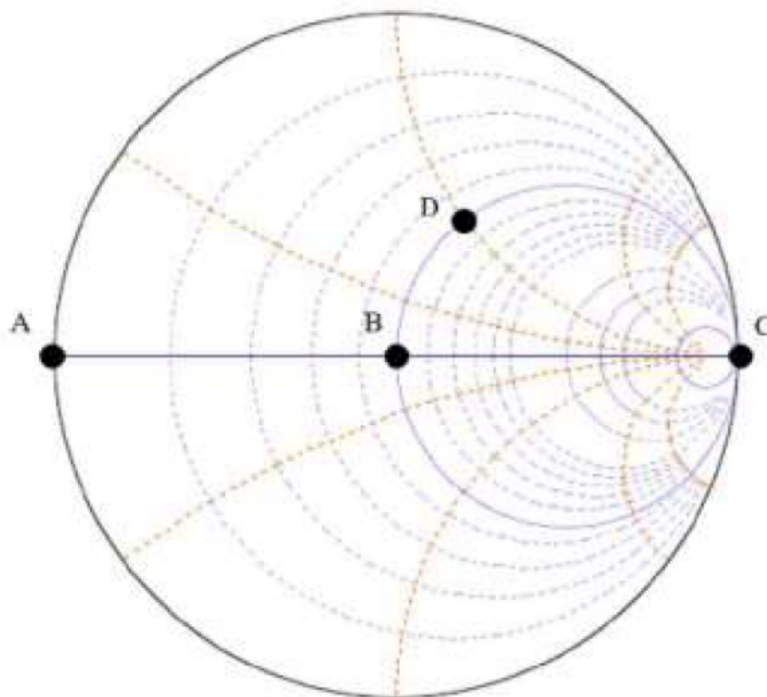Consider a transmission line of characteristic impedance $Z_0 = 50 \Omega$ terminated by a load impedance $Z_R = 0$. Which is the point of the normalized load impedance on Smith chart?




1. (A) A (B) B (C) C (D) D

Consider a transmission line of characteristic impedance $Z_0 = 50 \Omega$ terminated by a load impedance $Z_R = 50 \Omega$. Which is the point of the normalized load impedance in Smith chart?




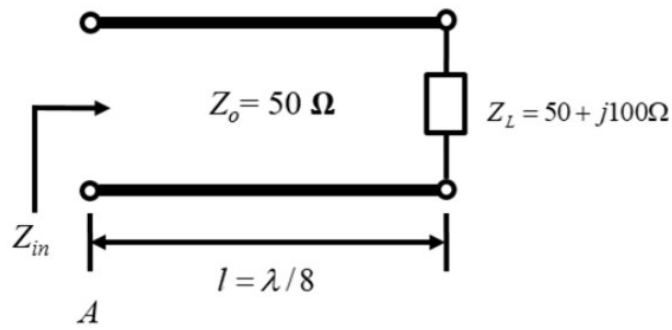
2. (A) A (B) B (C) C (D) D

For the system shown below, find the input impedance of the point A by using the Smith chart.



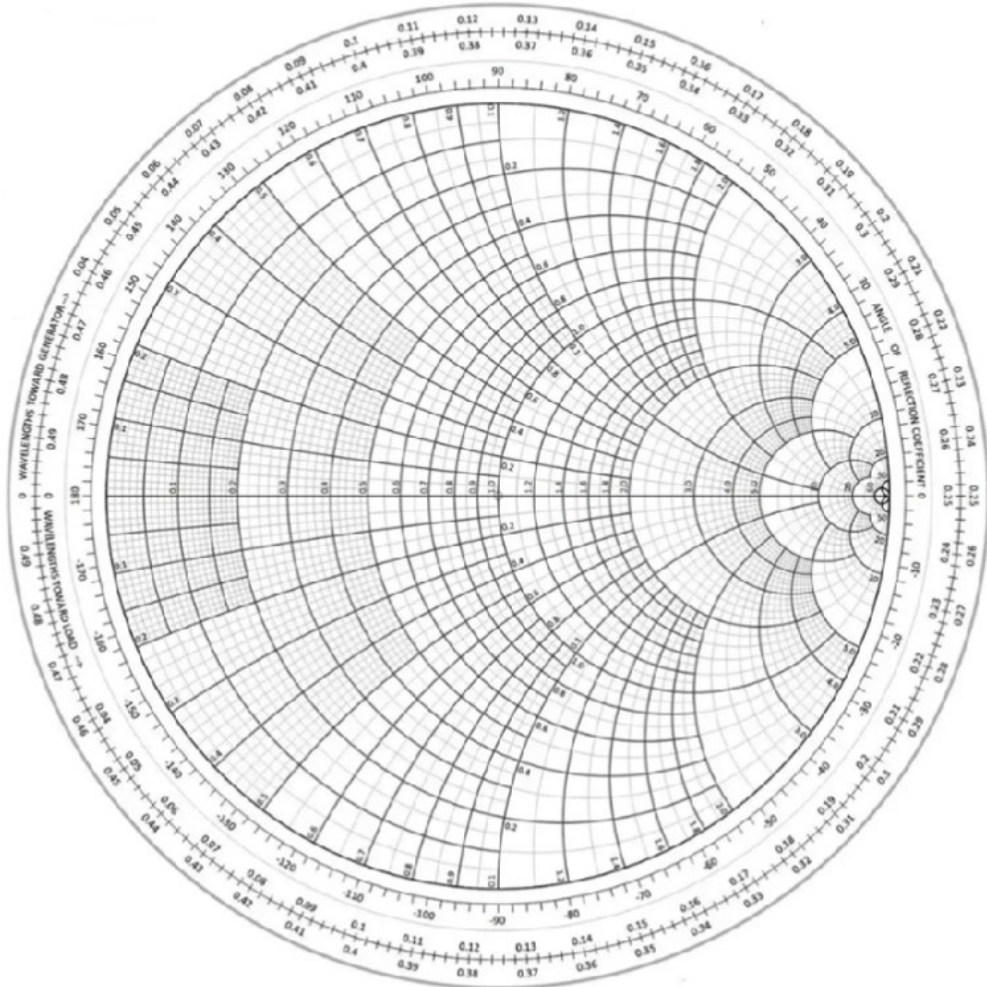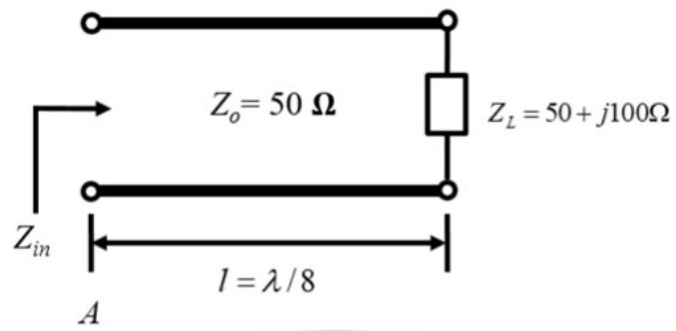3. (A) $50 - j 50 \Omega$ (B) $50 + j 50 \Omega$ (C) $50 - j 100 \Omega$ (D) $50 + j 100 \Omega$

For the system shown below, find the input admittance of the point A by using the Smith chart.



- (A) $4 + j8 \text{ mS}$
 (B) $2 + j5 \text{ mS}$
 (C) $4 - j8 \text{ mS}$
 (D) $2 - j5 \text{ mS}$

4.

Specify the regions on Smith chart for capacitive, inductive, and resistive loads, respectively.

(A) Upper semicircle: inductive; lower semicircle: resistive; real axis: capacitive



(B) Upper semicircle: inductive; lower semicircle: capacitive; real axis: resistive

(C) Upper semicircle: capacitive; lower semicircle: resistive; real axis: inductive

(D) Upper semicircle: capacitive; lower semicircle: inductive; real axis: resistive

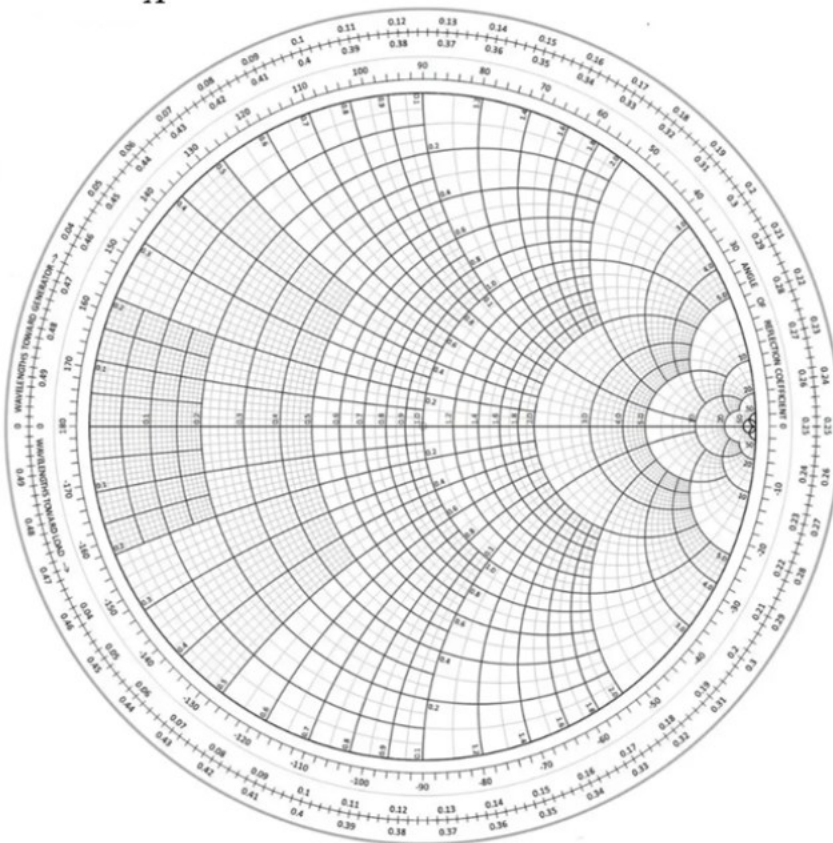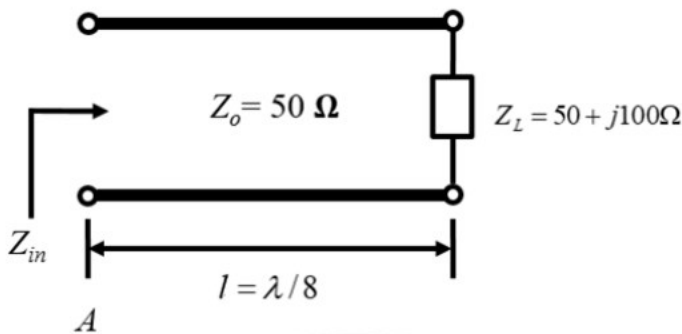5.



For the system shown below, find the reflection coefficient at the load by using the Smith chart.



6.

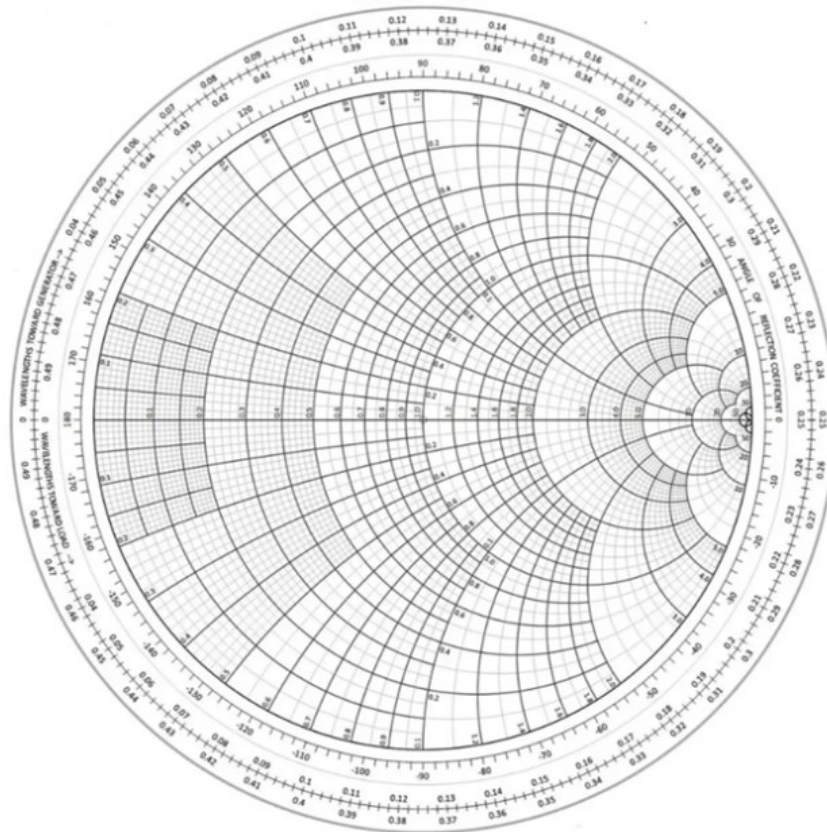
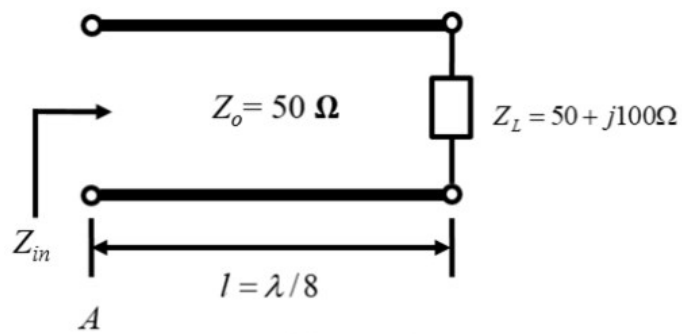
(A) $0.707 \angle 45^\circ$ (B) $0.707 \angle -45^\circ$ (C) $0.5 \angle 45^\circ$ (D) $0.5 \angle 135^\circ$

For the system shown below, find the standing wave ratio (SWR) on the line by using the Smith chart.



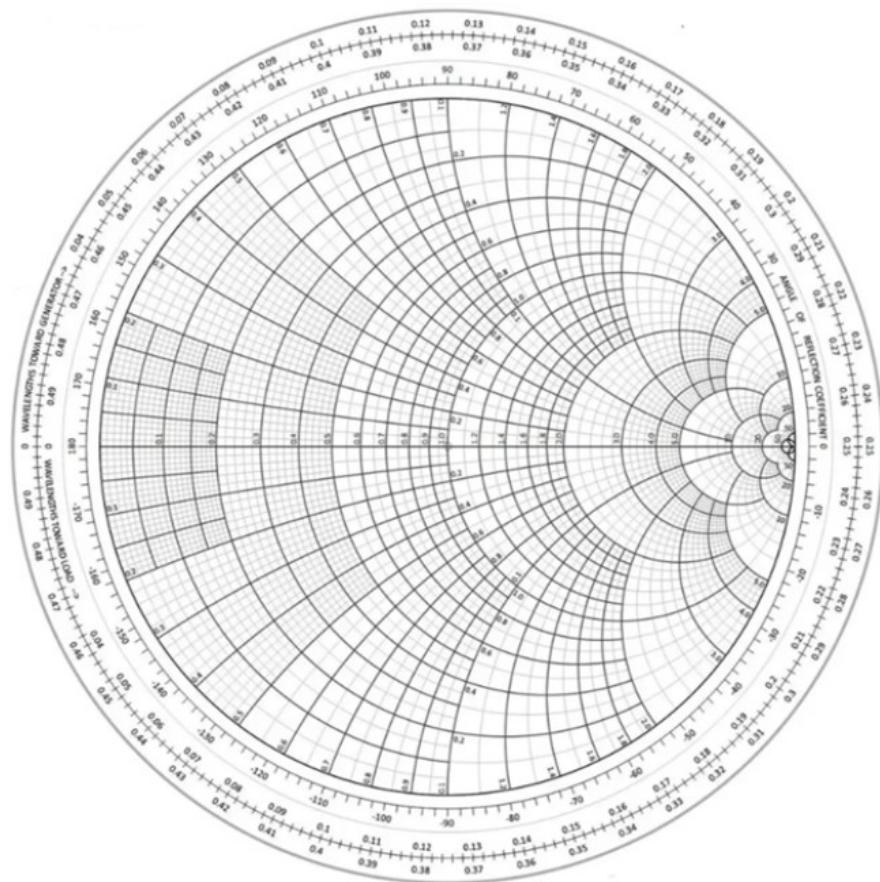
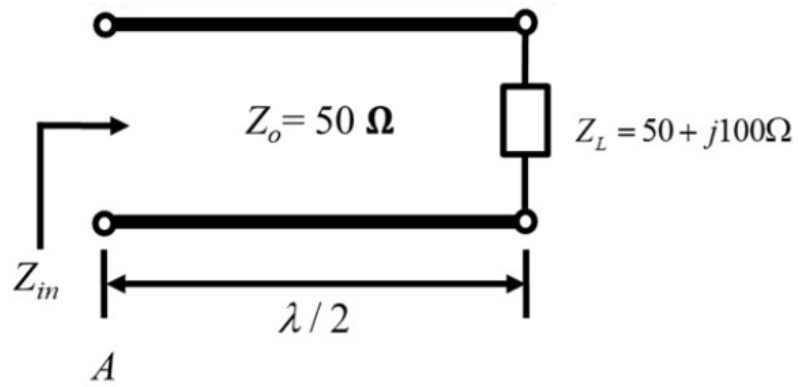
7. (A) 0.175 (B) 0.707 (C) 5.8 (D) 0

For the system shown below, find the distance ℓ_M between load and the point of maximum voltage wave by using the Smith chart.



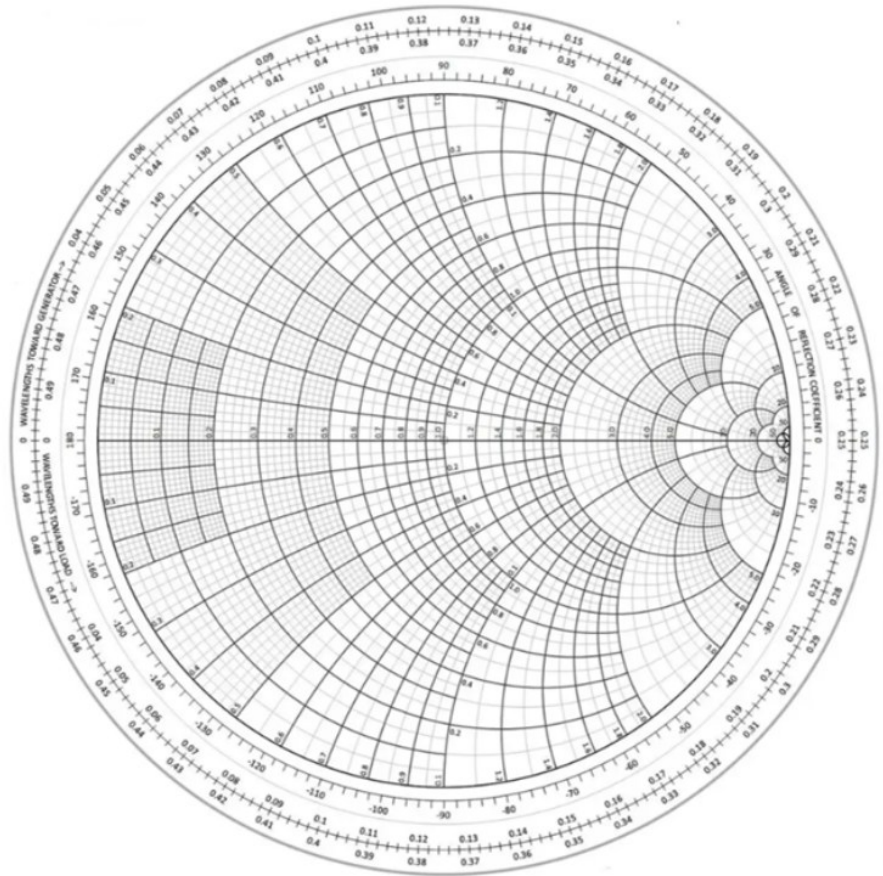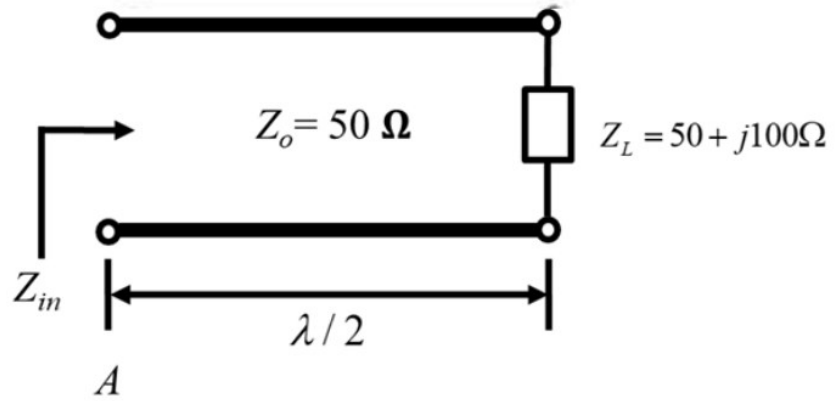8. (A) $\ell_M = 0.06\lambda$ (B) $\ell_M = 0.19\lambda$ (C) $\ell_M = 0.32\lambda$ (D) $\ell_M = 0.44\lambda$


For the system shown below, find the distance ℓ_m between load and the point of minimum voltage wave by using the Smith chart.



9.

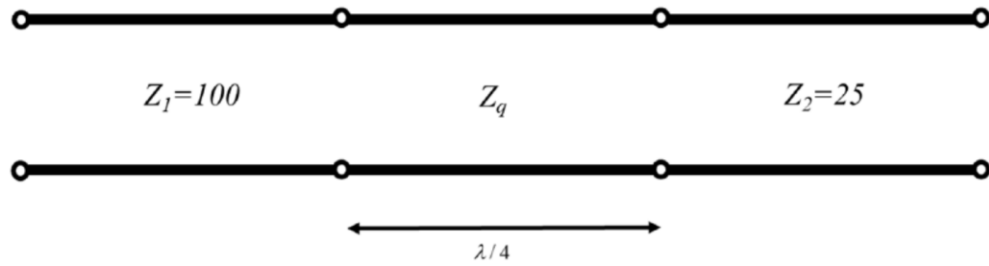- (A) $\ell_m = 0.06\lambda$ (B) $\ell_m = 0.19\lambda$ (C) $\ell_m = 0.31\lambda$ (D) $\ell_m = 0.44\lambda$

Two transmission lines are connected together, as shown below. Please use the quarter-wave length transformer to reduce the reflection to be zero and find the SWR at the matching transmission line section



(A) $Z_q = 50$; SWR=2


(B) $Z_q = 75$; SWR=2

(C) $Z_q = 50$; SWR=3

(D) $Z_q = 75$; SWR=3

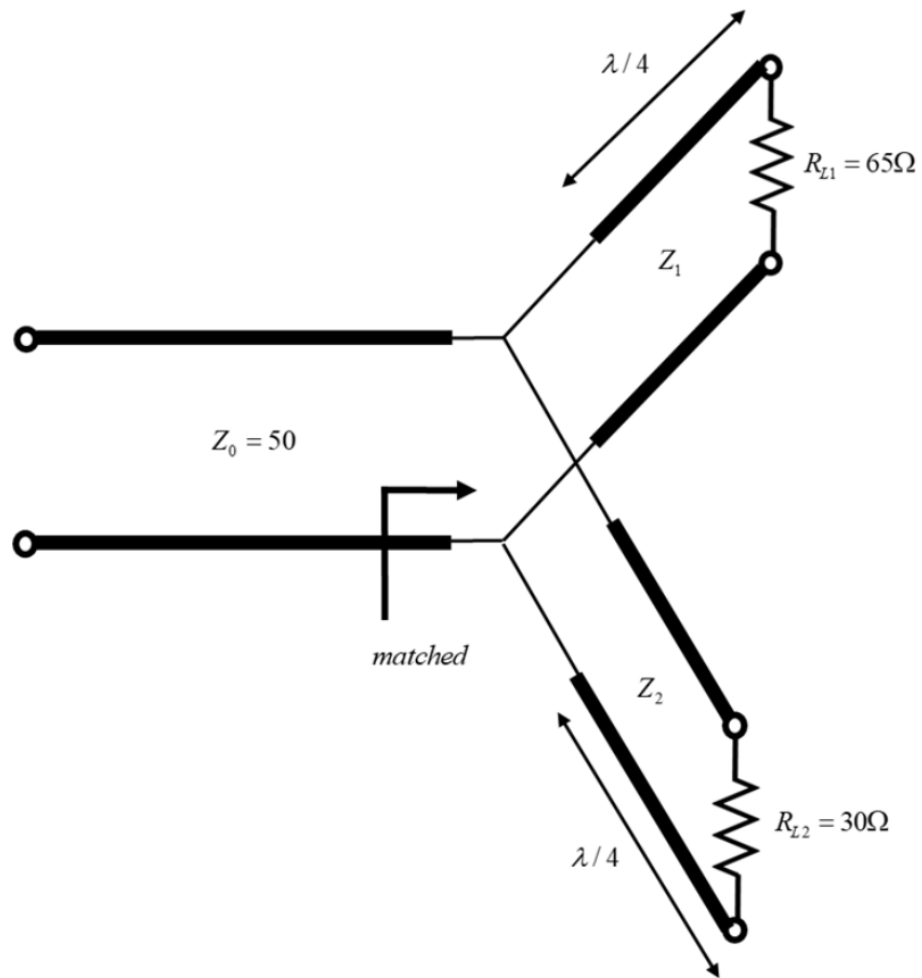10.


For the lossless system shown below, find the Z_1 and Z_2 so that the system is matched.



- (A) $Z_1 = 50.6\Omega$; $Z_2 = 54.8\Omega$
- (B) $Z_1 = 90.6\Omega$; $Z_2 = 54.8\Omega$
- (C) $Z_1 = 80.6\Omega$; $Z_2 = 54.8\Omega$
- (D) $Z_1 = 80.6\Omega$; $Z_2 = 90.6\Omega$

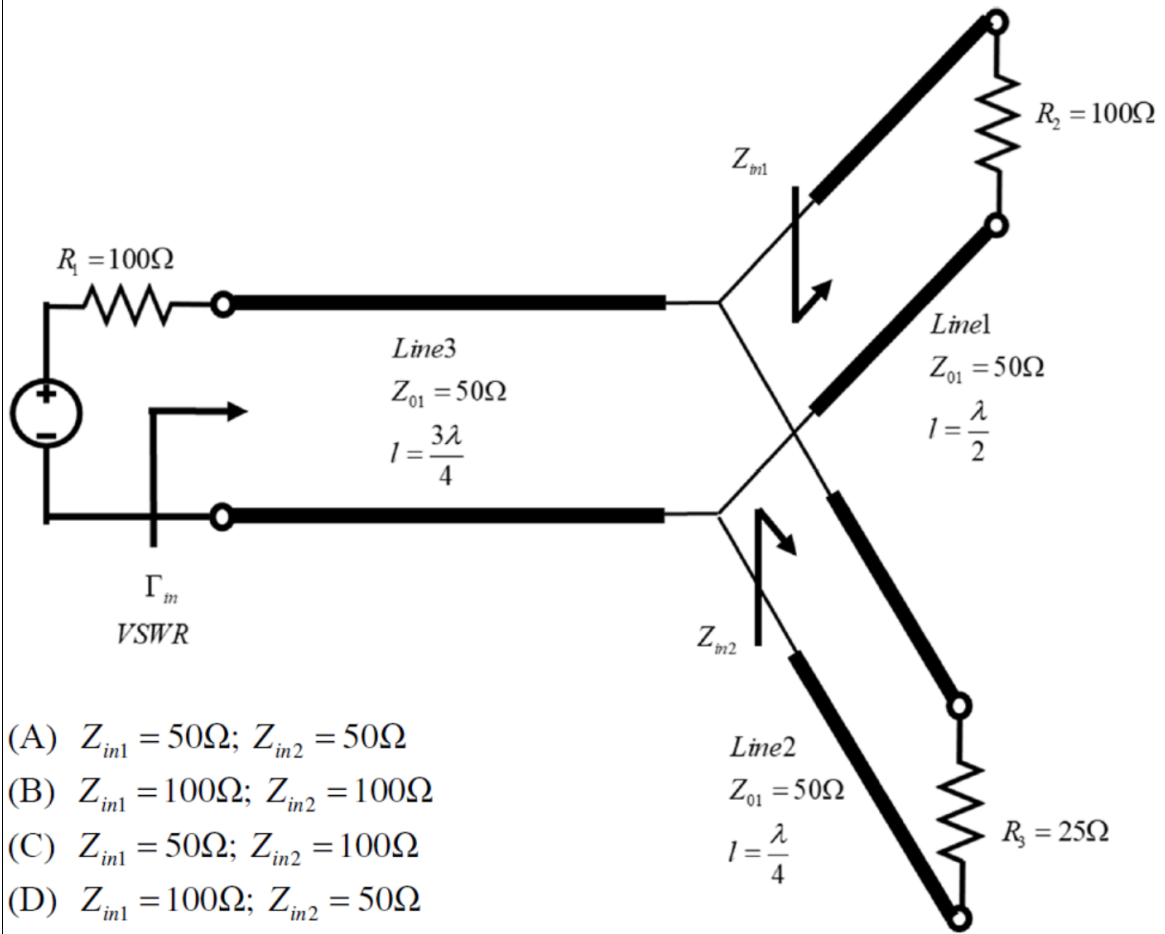11.

For the lossless transmission system shown below, find the input impedance Z_{in1} and Z_{in2} .




- (A) $Z_{in1} = 50\Omega$; $Z_{in2} = 50\Omega$
 (B) $Z_{in1} = 100\Omega$; $Z_{in2} = 100\Omega$
 (C) $Z_{in1} = 50\Omega$; $Z_{in2} = 100\Omega$
 (D) $Z_{in1} = 100\Omega$; $Z_{in2} = 50\Omega$

12.

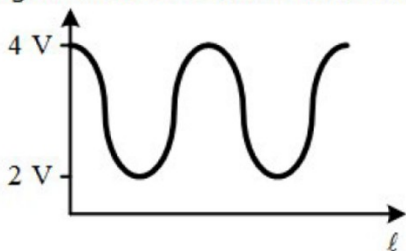13.


The measured standing-wave pattern of a finite transmission line terminated with load impedance Z_L is shown in the below figure. Determine which answer listed in the following is its corresponding standing-wave ratio?



- (1) $SWR = 2$
 (2) $SWR = 1$
 (3) $SWR = \infty$

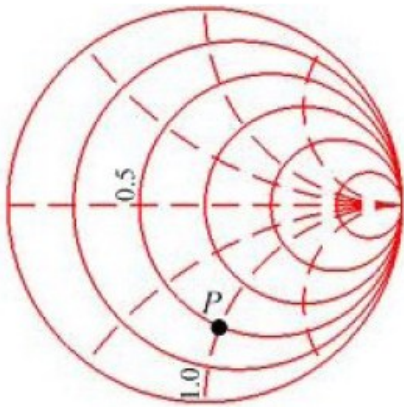14.


What is the impedance of the point P on the Smith chart, as shown in the figure ?
The reference impedance Z_0 is 50Ω



- (1) $25 + j25 \Omega$
- (2) $25 + j50 \Omega$
- (3) $25 - j50 \Omega$
- (4) $50 - j25 \Omega$
- (5) $50 + j25 \Omega$

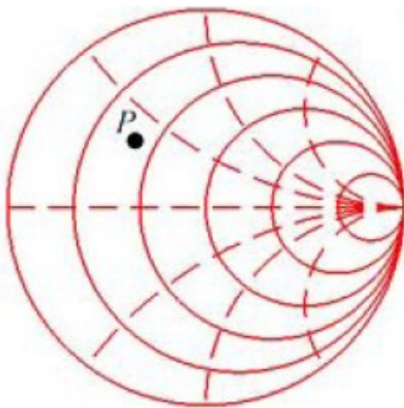15.

A lumped circuit represented by the point P on the Smith chart, as shown in the figure, is most likely to be




- (1) an inductor
- (2) a capacitor
- (3) a resistor
- (4) an RL circuit
- (5) an RC circuit

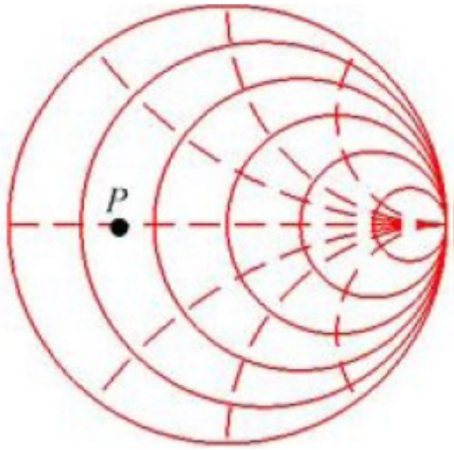16.

What does the point P on the Smith chart represent, as shown in the figure?

The impedance is normalized to $50\ \Omega$. ↵



- (1) a short circuit
- (2) an open circuit
- (3) a $17\ \Omega$ resistor
- (4) a $147\ \Omega$ resistor
- (5) a reactive circuit ↵

17.

Why is the impedance matching important for microwave circuits design?

- (1) Just for fun
- (2) For a maximum voltage transfer to the load
- (3) For a maximum current transfer to the load
- (4) For a maximum power transfer to the load
- (5) For a maximum noise transfer to the load ↵


18.

The figure shows a single – stub matching circuit used to match a load to a lossless transmission line of Z_0 .

Which one of the following statements is true?

- (1) A purely resistive load can not be matched by using the single-stub matching circuit.
- (2) A purely reactive load can not be matched by using the single-stub matching circuit.
- (3) A lump RL load can not be matched by using the single-stub matching circuit.
- (4) A lump RC load can not be matched by using the single-stub matching circuit.
- (5) A load of impedance $Z_L = Z_0$ can not be matched by using the single-stub matching circuit.

19.

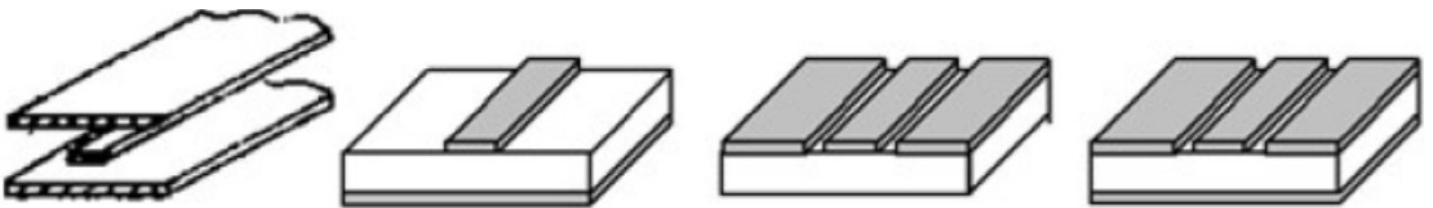

- (1) stripline 、 microstrip 、 CPW 、 grounded CPW
- (2) microstrip 、 stripline 、 CPW 、 grounded CPW
- (3) stripline 、 microstrip 、 grounded CPW 、 CPW
- (4) microstrip 、 stripline 、 grounded CPW 、 CPW

20.

一條傳輸線的終端連接一負載阻抗，若反射係數為 $0.8\angle 45^\circ$ ，且波長為30 cm，則最接近負載之電壓最小值的位置為何？

- (1) 2.9 cm
- (2) 5.7 cm
- (3) 9.4 cm
- (4) 11.2 cm

A TL with a load, and its reflection at the load is $0.8\angle 45^\circ$. The wavelength is **30 cm**. Where is the **nearest V_{\min}** position from the load?